

## Practical 3

### Controlling the LED blink rate with the potentiometer interfacing with Arduino

**Introduction:** A potentiometer is a variable resistor with a knob that allows altering the resistance of the potentiometer. The potentiometer manipulates a continuous analog signal, which represents physical measurements. The potentiometer is used with Arduino to control the blink rate of the LED. The potentiometer is an adjustable resistor, and its operating principle is shown in the following figure:




#### **Hardware Required:**

Component	Quantity
Arduino Uno	1
Bread board	1
220 $\Omega$ current limiting resistor	1

5mm LED	1
10K $\Omega$ Potentiometer	1
Jumper Wires	Several
Supporting USB data cable	1

### Working Diagram:

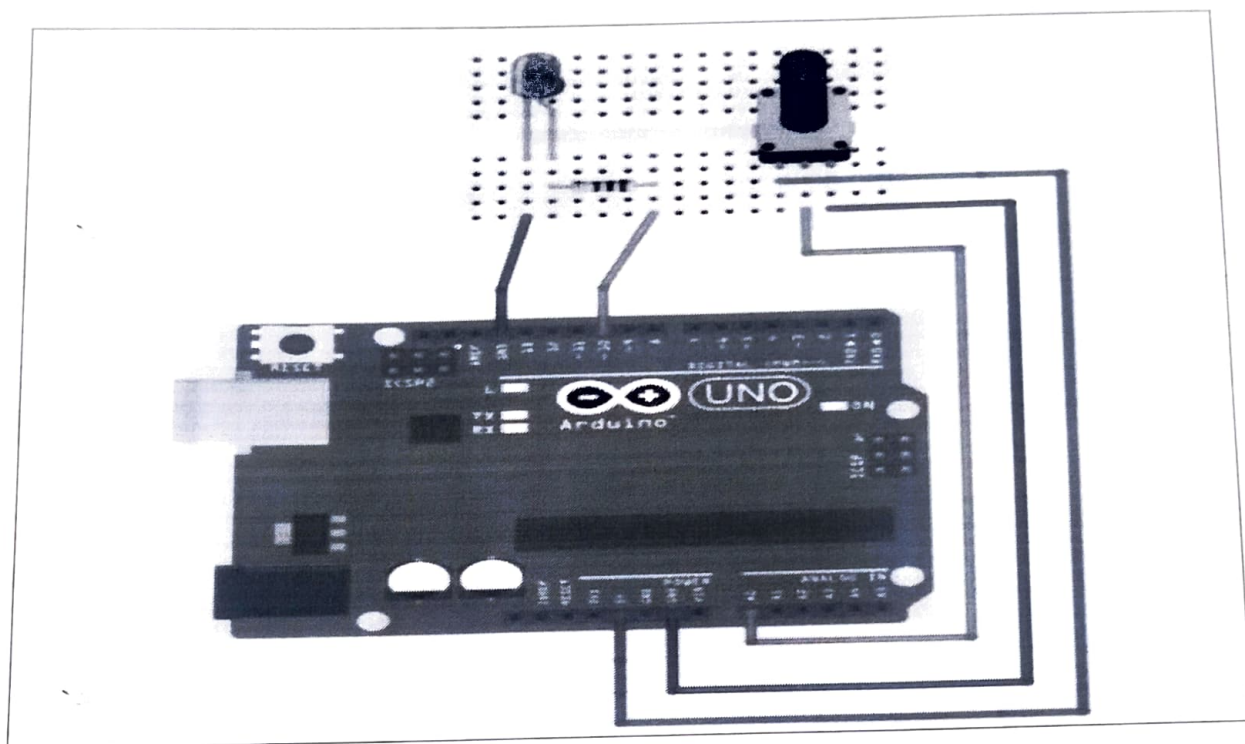

### Steps of working

1. Insert the potentiometer into your breadboard and connect its center pin to the analog pin A2 and the remaining pin to GND on the breadboard.

5. Observe the changes in the blinking rate of the LED.

### The Sketch

The voltage value is between 0–5 volts, and the brightness of the LED will vary accordingly.

Observation Table:

Sr. no.	Voltage	Light Intensity
1		
2		
3		
4		
5		